

Multi-cycle MIPS Processor

Design of Digital Circuits 2014

Srdjan Capkun

Frank K. Gürkaynak

http://www.syssec.ethz.ch/education/Digitaltechnik_14


What Will We Learn?

- **What are the problems of Single-cycle Processor**
- **Multi-cycle Architecture for the MIPS**
- **Determine the performance of Multi-cycle Processor**

Single-cycle MIPS Processor

- **Single-cycle microarchitecture:**
 - + simple
 - cycle time limited by longest instruction (1w)
 - two adders/ALUs and two memories

Single-cycle Performance

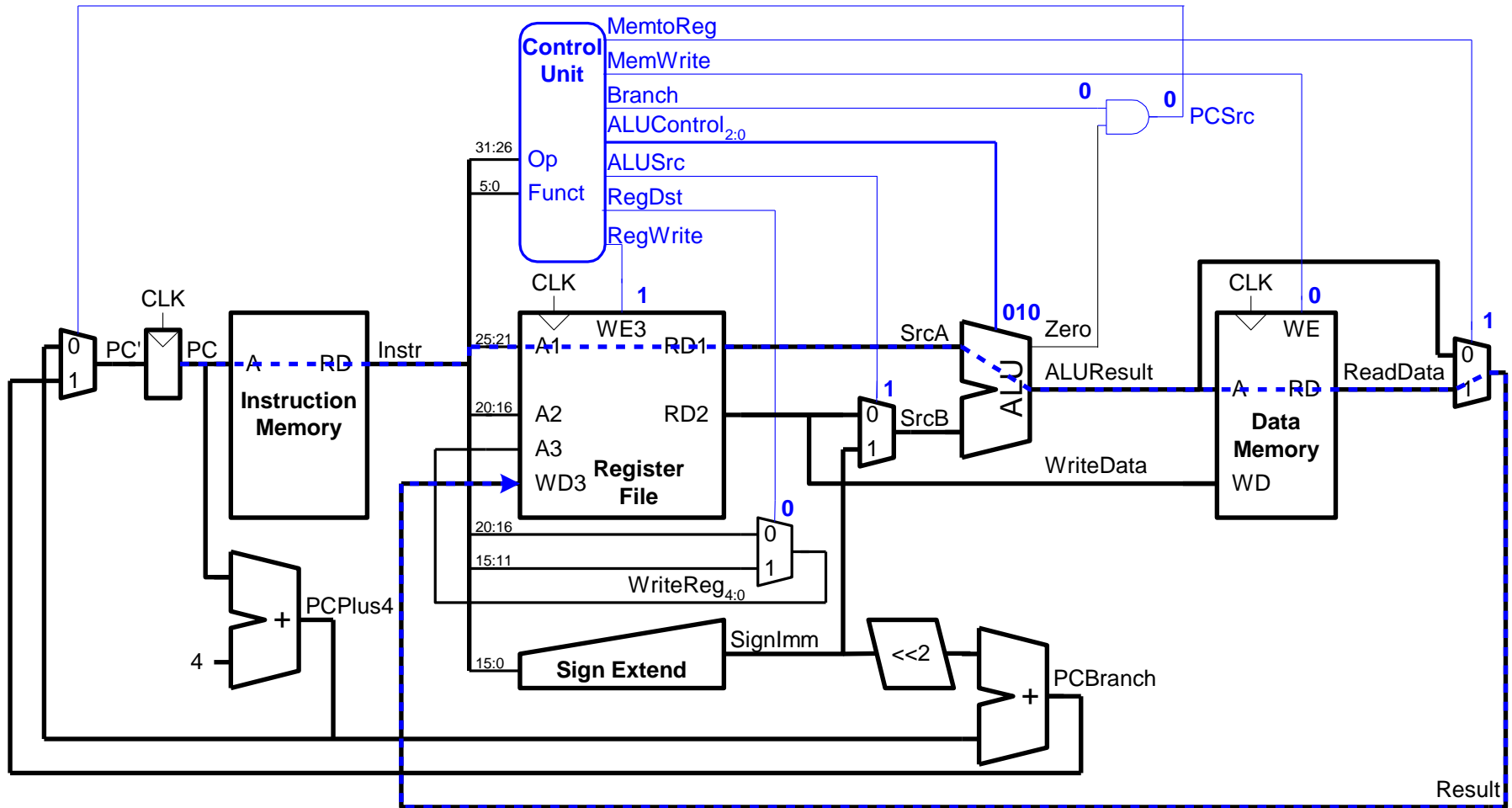

Delay of Individual Components (Example)

| Element | Parameter | Delay (ps) |
|---------------------------|--------------------------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| <i>ALU</i> | <i>t_{ALU}</i> | <i>200</i> |
| <i>Memory read</i> | <i>t_{mem}</i> | <i>250</i> |
| <i>Register file read</i> | <i>t_{RFread}</i> | <i>150</i> |
| Register file setup | $t_{RFsetup}$ | 20 |

Processor Performance

■ How fast is my program?

- Every program consists of a series of instructions
- Each instruction needs to be executed.

■ So how fast are my instructions ?

- Instructions are realized on the hardware
- They can take one or more clock cycles to complete
- *Cycles per Instruction = CPI*

■ How much time is one clock cycle?

- The critical path determines how much time one cycle requires = *clock period*.
- $1/\text{clock period} = \text{clock frequency}$ = how many cycles can be done each second.

Processor Performance

■ Now as a general formula

- Our program consists of executing **N** instructions.
- Our processor needs **CPI** cycles for each instruction.
- The maximum clock speed of the processor is **f**, and the clock period is therefore **T=1/f**

■ Our program will execute in

$$\mathbf{N \times CPI \times (1/f) = N \times CPI \times T \text{ seconds}}$$

How can I Make the Program Run Faster?

$$N \times \text{CPI} \times (1/f)$$

- **Reduce the number of instructions**
 - Make instructions that 'do' more (CISC)
 - Use better compilers
- **Use less cycles to perform the instruction**
 - Simpler instructions (RISC)
 - Use multiple units/ALUs/cores in parallel
- **Increase the clock frequency**
 - Find a 'newer' technology to manufacture
 - Redesign time critical components
 - Adopt pipelining

Multi-cycle MIPS Processor

■ Single-cycle microarchitecture:

- + simple
- cycle time limited by longest instruction (lw)
- two adders/ALUs and two memories

■ Multi-cycle microarchitecture:

- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times

■ Same design steps: datapath & control

What Do We Want To Optimize

- **Single Cycle Architecture uses two memories**
 - One memory stores instructions, the other data
 - We want to use a single memory (Smaller size)

What Do We Want To Optimize

- **Single Cycle Architecture uses two memories**
 - One memory stores instructions, the other data
 - We want to use a single memory (Smaller size)
- **Single Cycle Architecture needs three adders**
 - ALU, PC, Branch address calculation
 - We want to use the ALU for all operations (smaller size)

What Do We Want To Optimize

- **Single Cycle Architecture uses two memories**
 - One memory stores instructions, the other data
 - We want to use a single memory (Smaller size)
- **Single Cycle Architecture needs three adders**
 - ALU, PC, Branch address calculation
 - We want to use the ALU for all operations (smaller size)
- **In Single Cycle Architecture all instructions take one cycle**
 - The most complex operation slows down everything!
 - Divide all instructions into multiple steps
 - Simpler instructions can take fewer cycles (average case may be faster)


Consider lw instruction

- For an instruction such as: `lw $t0, 0x20($t1)`
- We need to:
 - Read the instruction from memory
 - Then read `$t1` from register array
 - Add the immediate value (`0x20`) to calculate the memory address
 - Read the content of this address
 - Write to the register `$t0` this content

Multi-cycle Datapath: instruction fetch

■ First consider executing lw

■ STEP 1: Fetch instruction

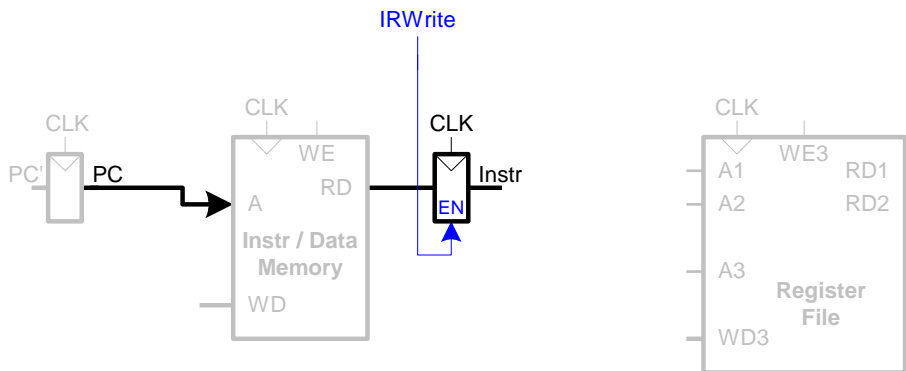


read from the memory location $[rs] + imm$ to location $[rt]$

I-Type

| | | | |
|--------|--------|--------|---------|
| op | rs | rt | imm |
| 6 bits | 5 bits | 5 bits | 16 bits |


Multi-cycle Datapath: lw register read

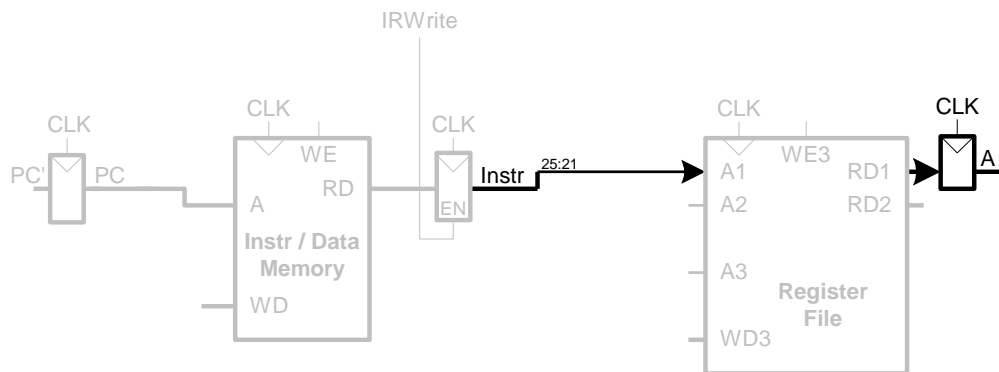

I-Type

| op | rs | rt | imm |
|--------|--------|--------|---------|
| 6 bits | 5 bits | 5 bits | 16 bits |


Multi-cycle Datapath: lw immediate

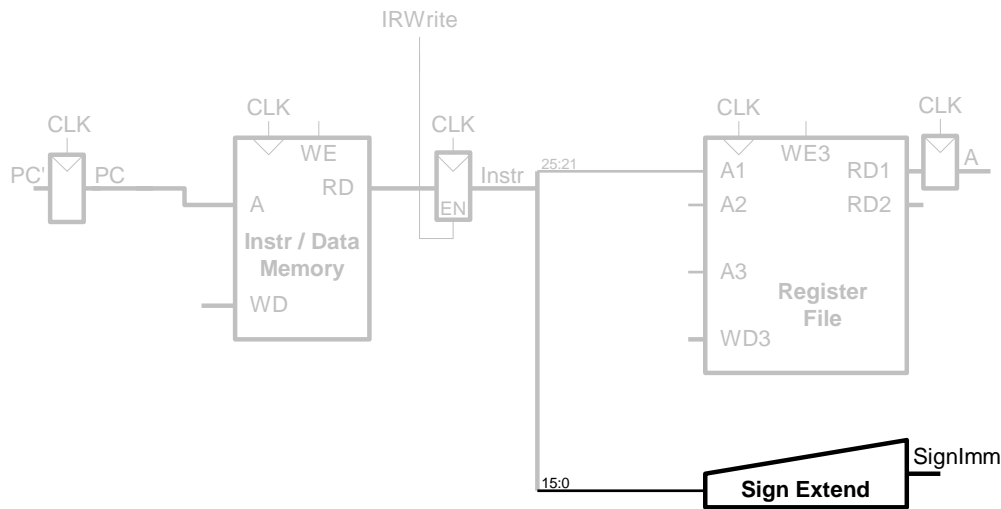

I-Type

| | | | |
|--------|--------|--------|---------|
| op | rs | rt | imm |
| 6 bits | 5 bits | 5 bits | 16 bits |


Multi-cycle Datapath: lw address

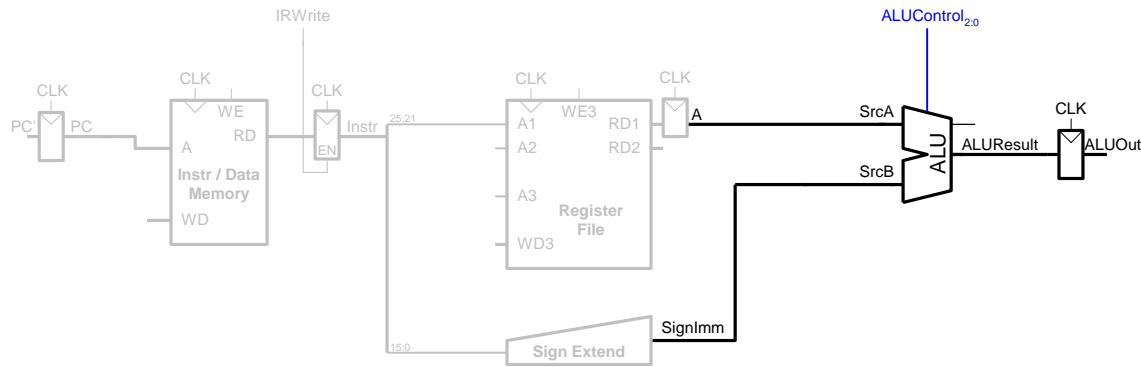

I-Type

| | | | |
|--------|--------|--------|---------|
| op | rs | rt | imm |
| 6 bits | 5 bits | 5 bits | 16 bits |


Multi-cycle Datapath: lw memory read

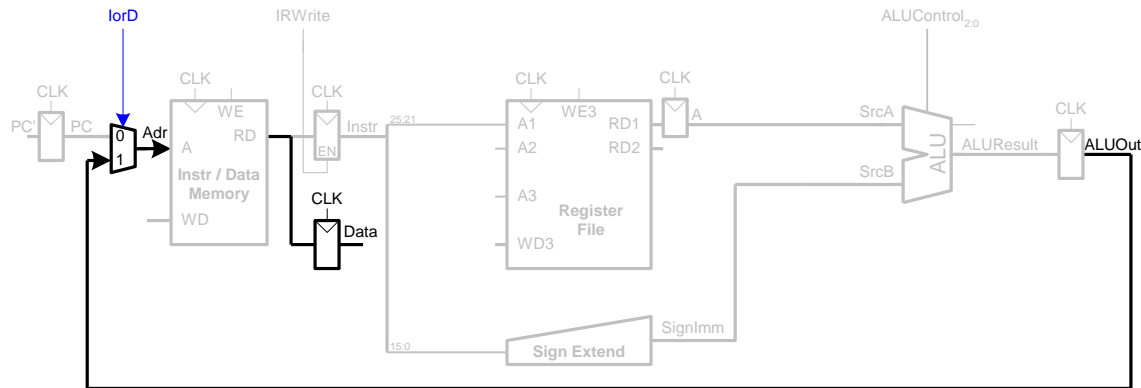

I-Type

| op | rs | rt | imm |
|--------|--------|--------|---------|
| 6 bits | 5 bits | 5 bits | 16 bits |


Multi-cycle Datapath: lw write register

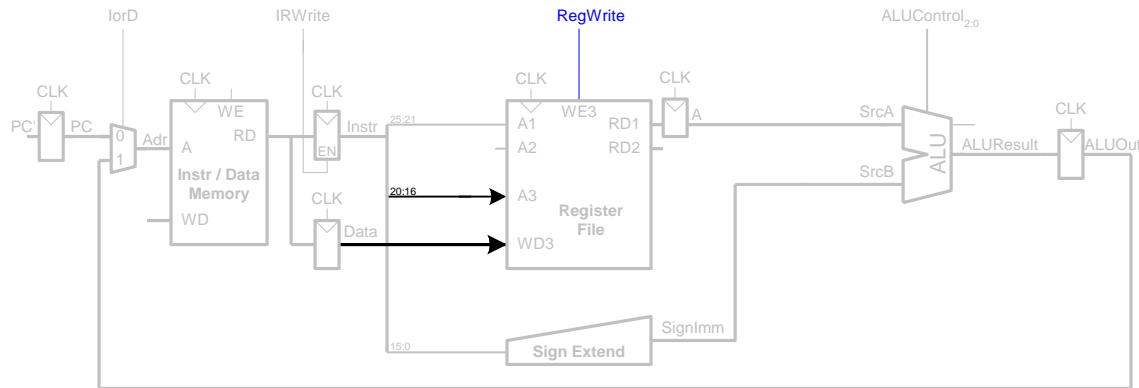

I-Type


| op | rs | rt | imm |
|--------|--------|--------|---------|
| 6 bits | 5 bits | 5 bits | 16 bits |

Multi-cycle Datapath: increment PC

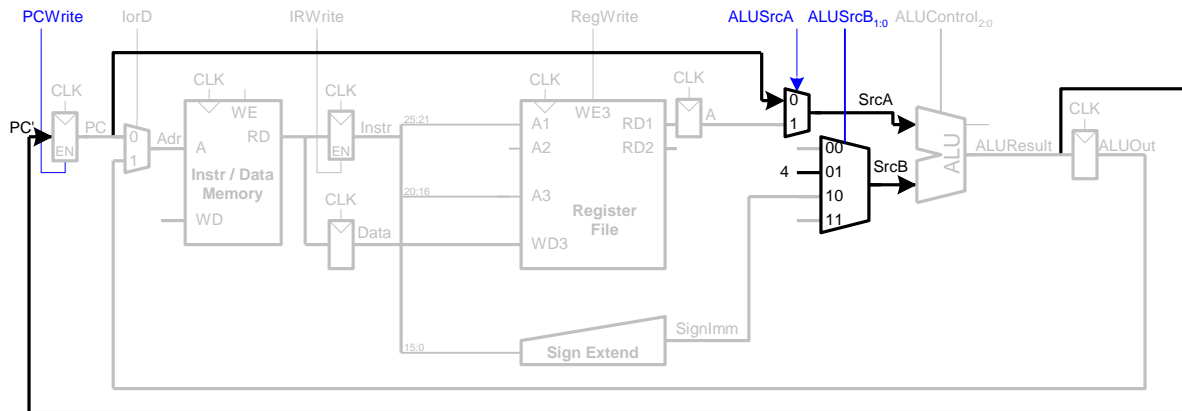


Multi-cycle Datapath: sw

■ Write data in rt to memory

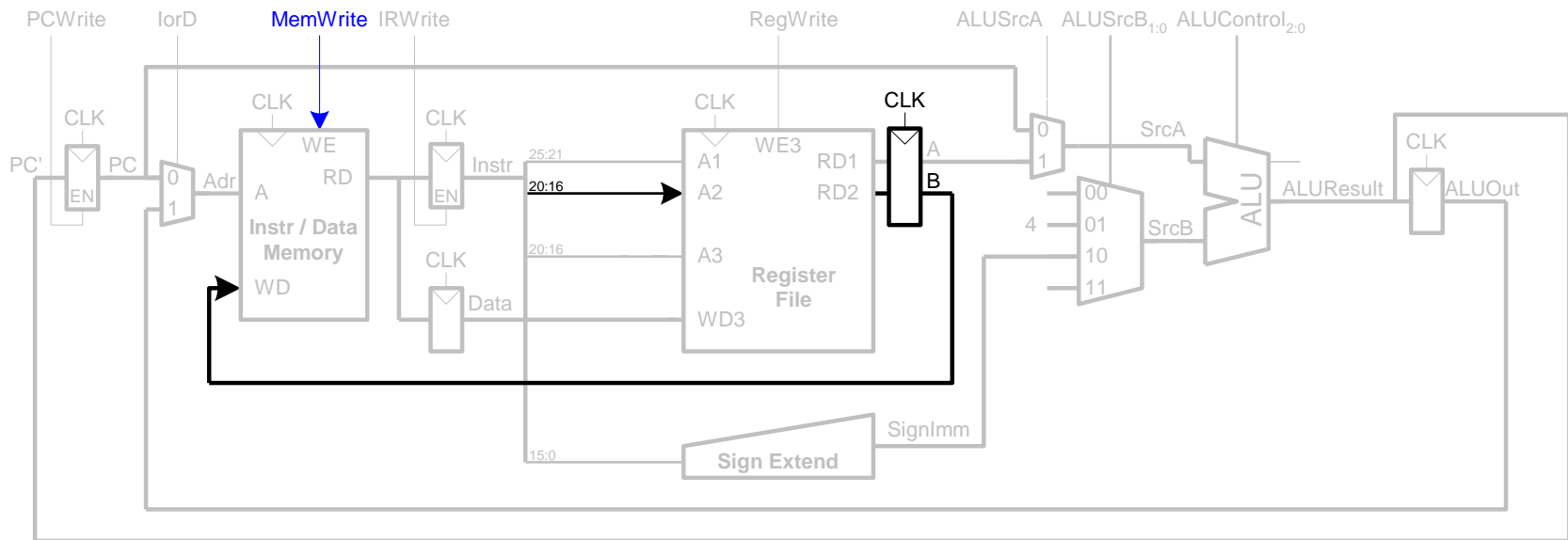

Multi-cycle Datapath: R-type Instructions

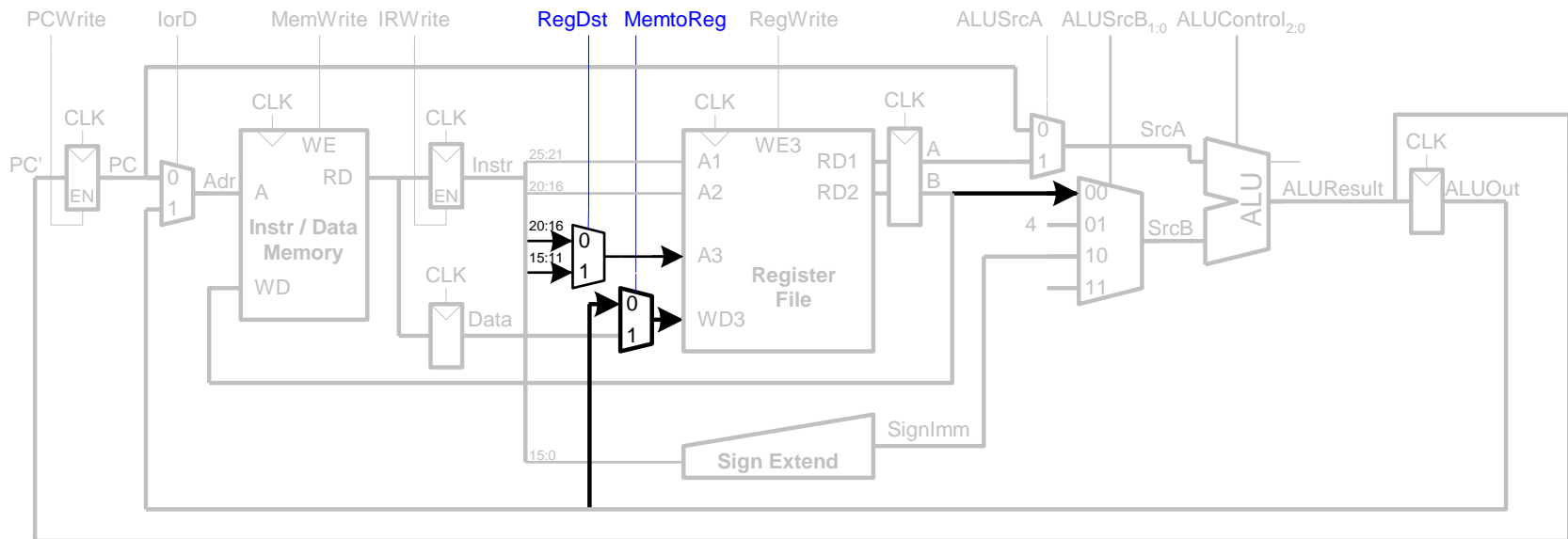- Read from rs and rt
 - Write ALUResult to register file
 - Write to rd (instead of rt)




Multi-cycle Datapath: beq


- Determine whether values in rs and rt are equal

- Calculate branch target address:

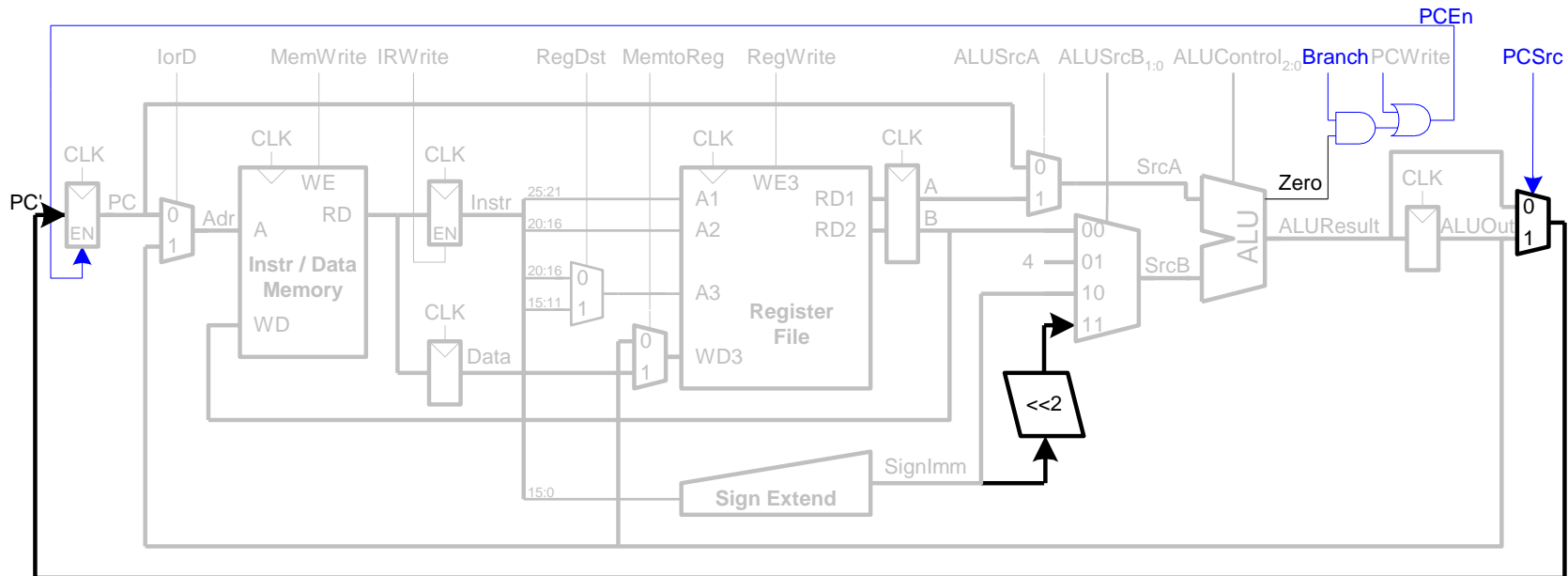
BTA = (sign-extended immediate << 2) + (PC+4)



Complete Multi-cycle Processor

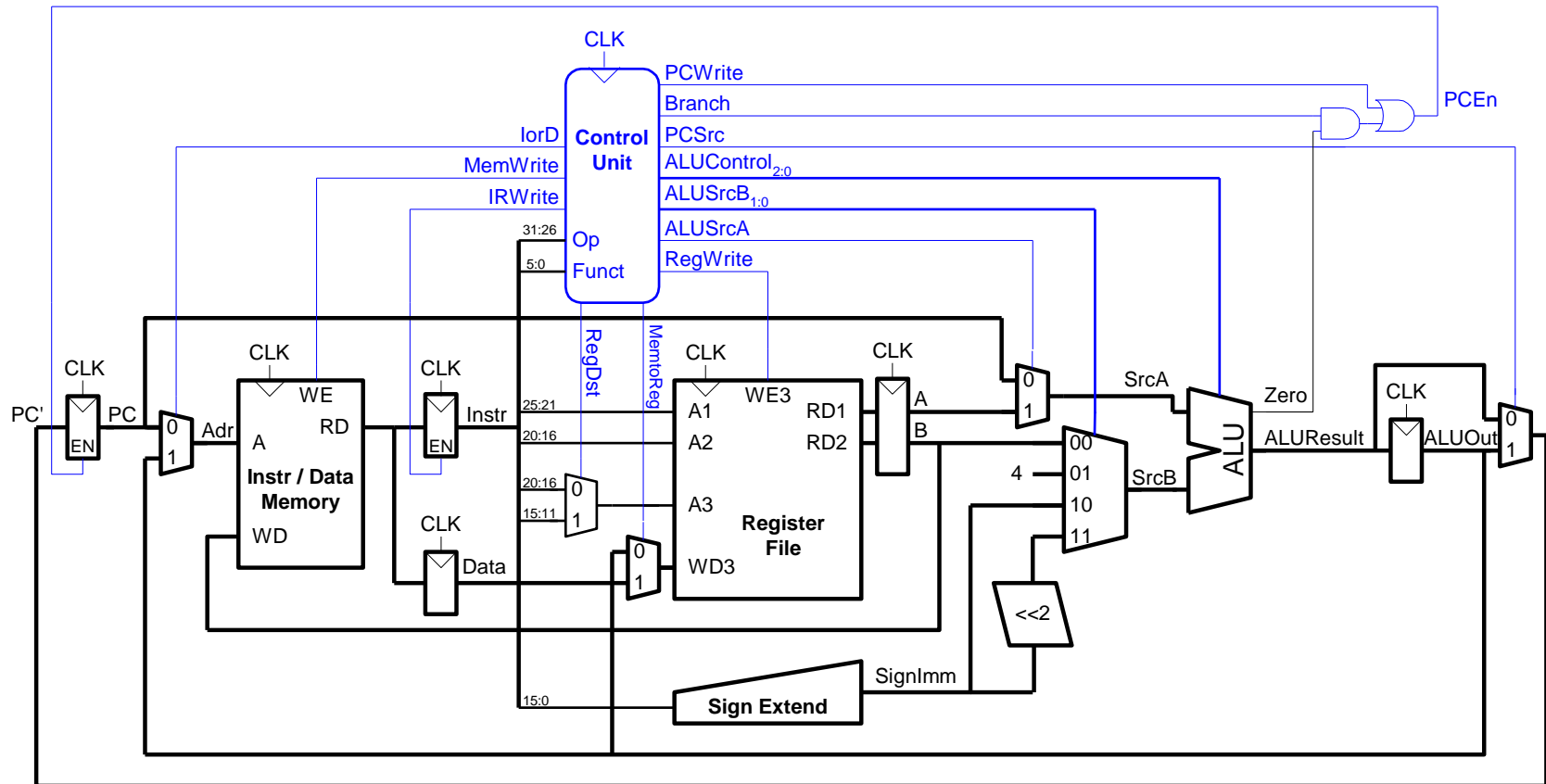


Control Unit

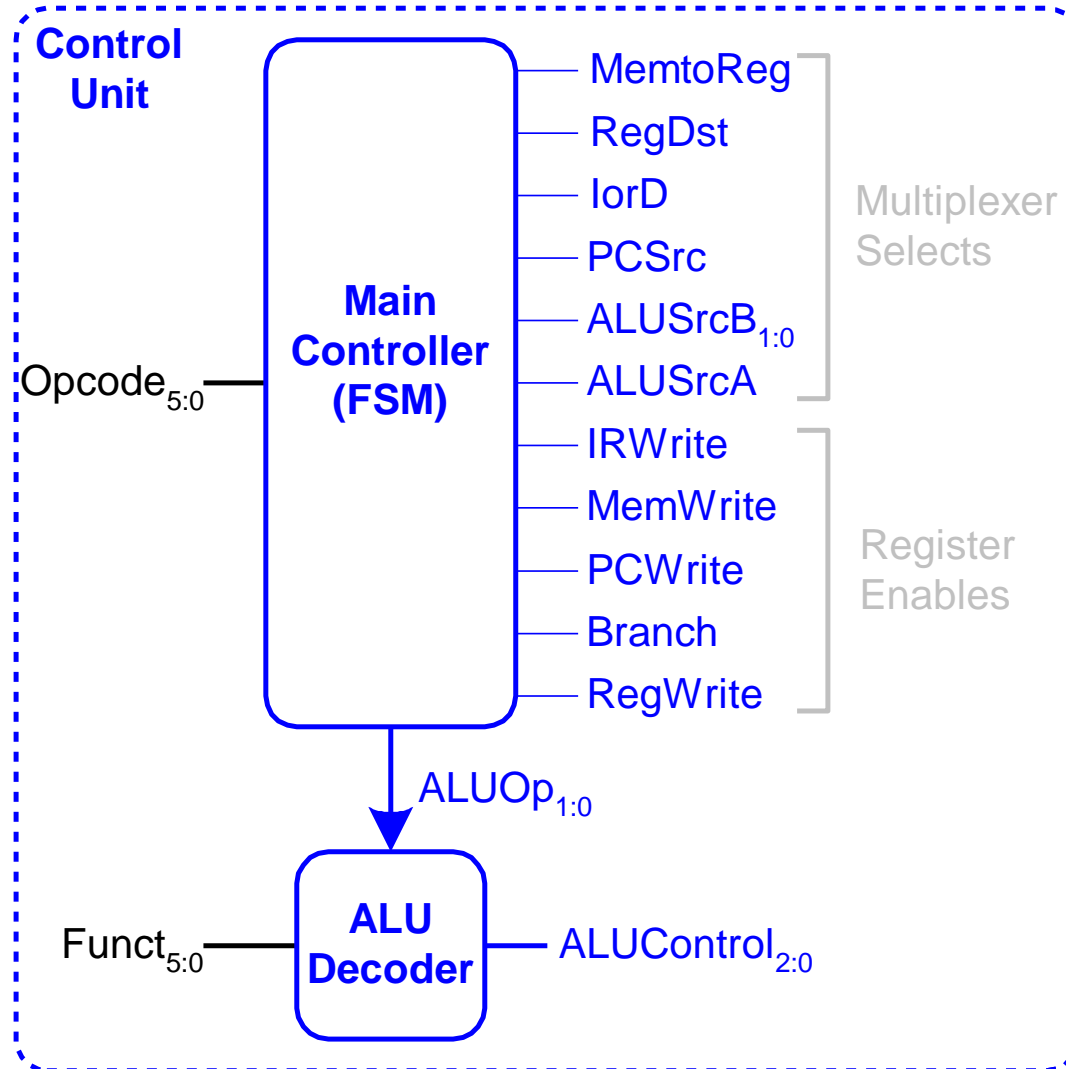

Main Controller FSM: Fetch

S0: Fetch

Reset

 


Main Controller FSM: Fetch

S0: Fetch

Reset


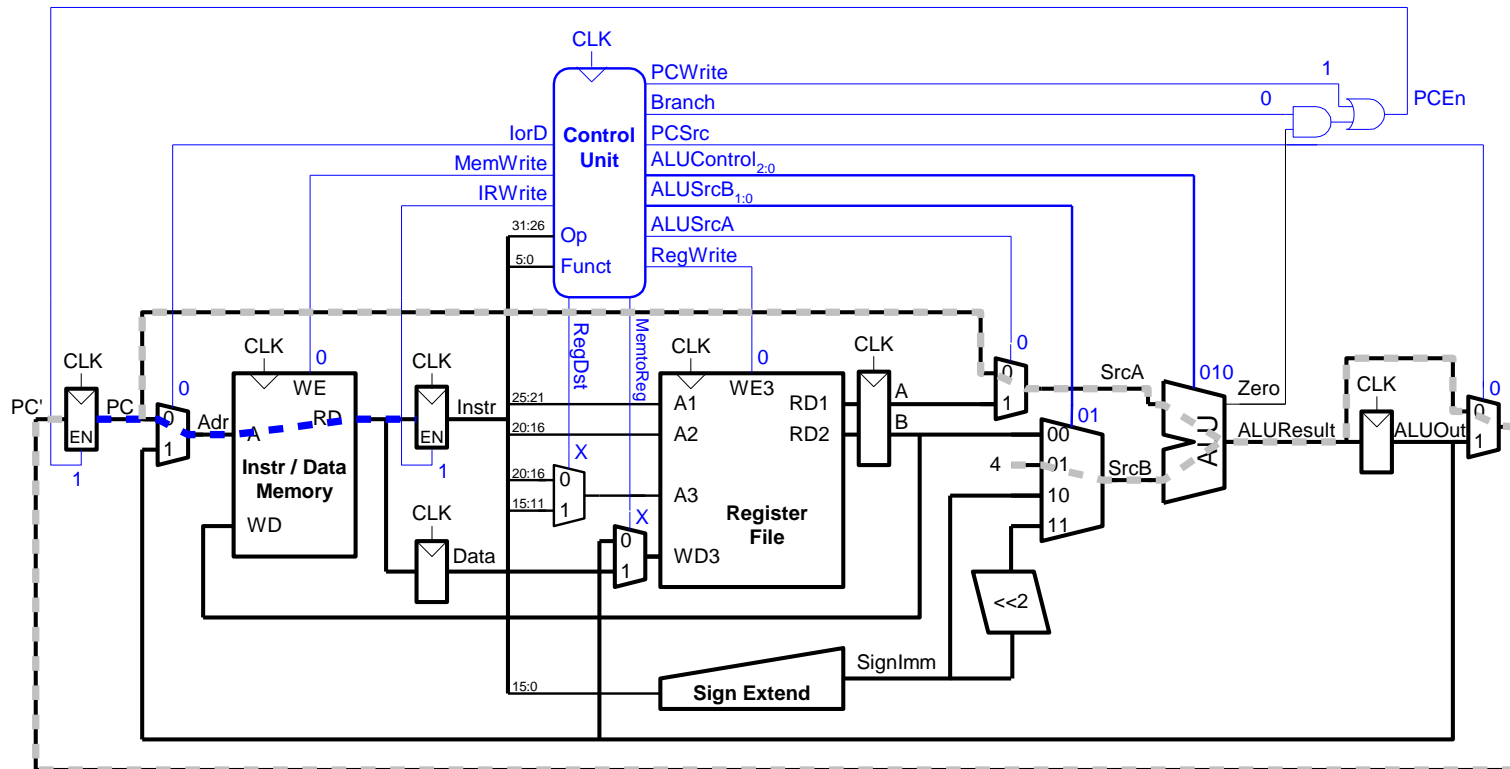
lorD = 0
AluSrcA = 0
ALUSrcB = 01
ALUOp = 00
PCSrc = 0
IRWrite
PCWrite




Main Controller FSM: Decode

S0: Fetch


S1: Decode

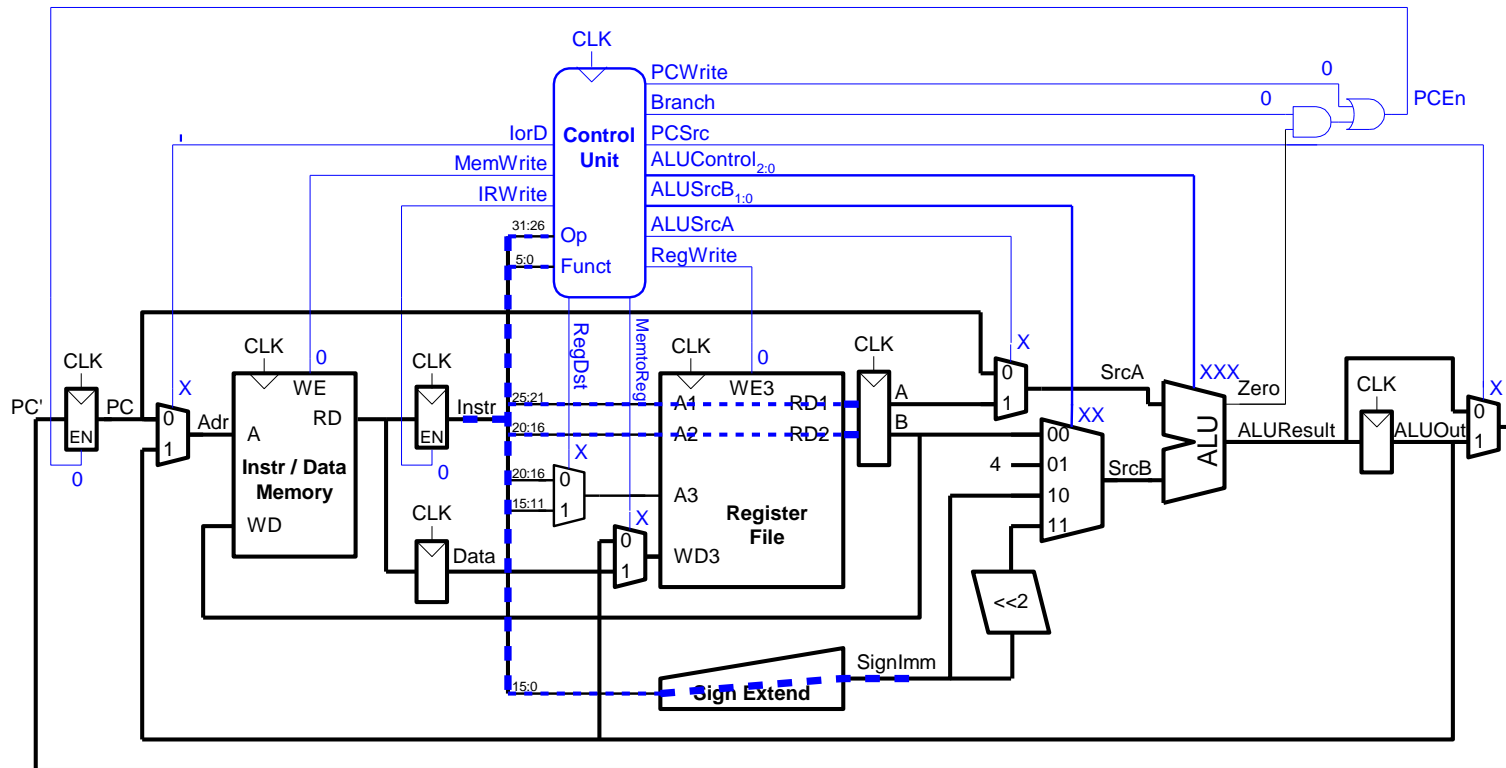 


Main Controller FSM: Address Calculation

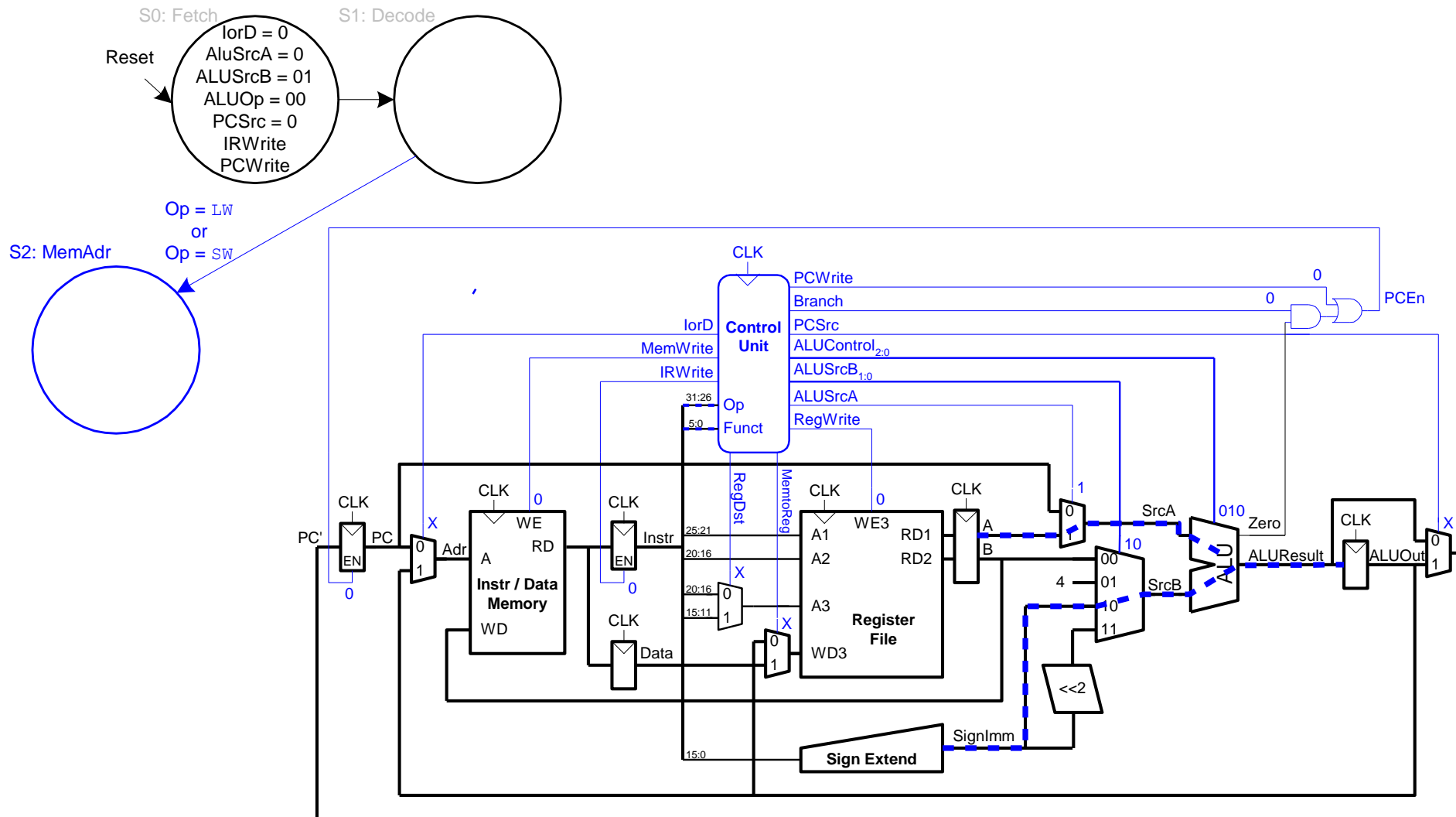


Main Controller FSM: Address Calculation

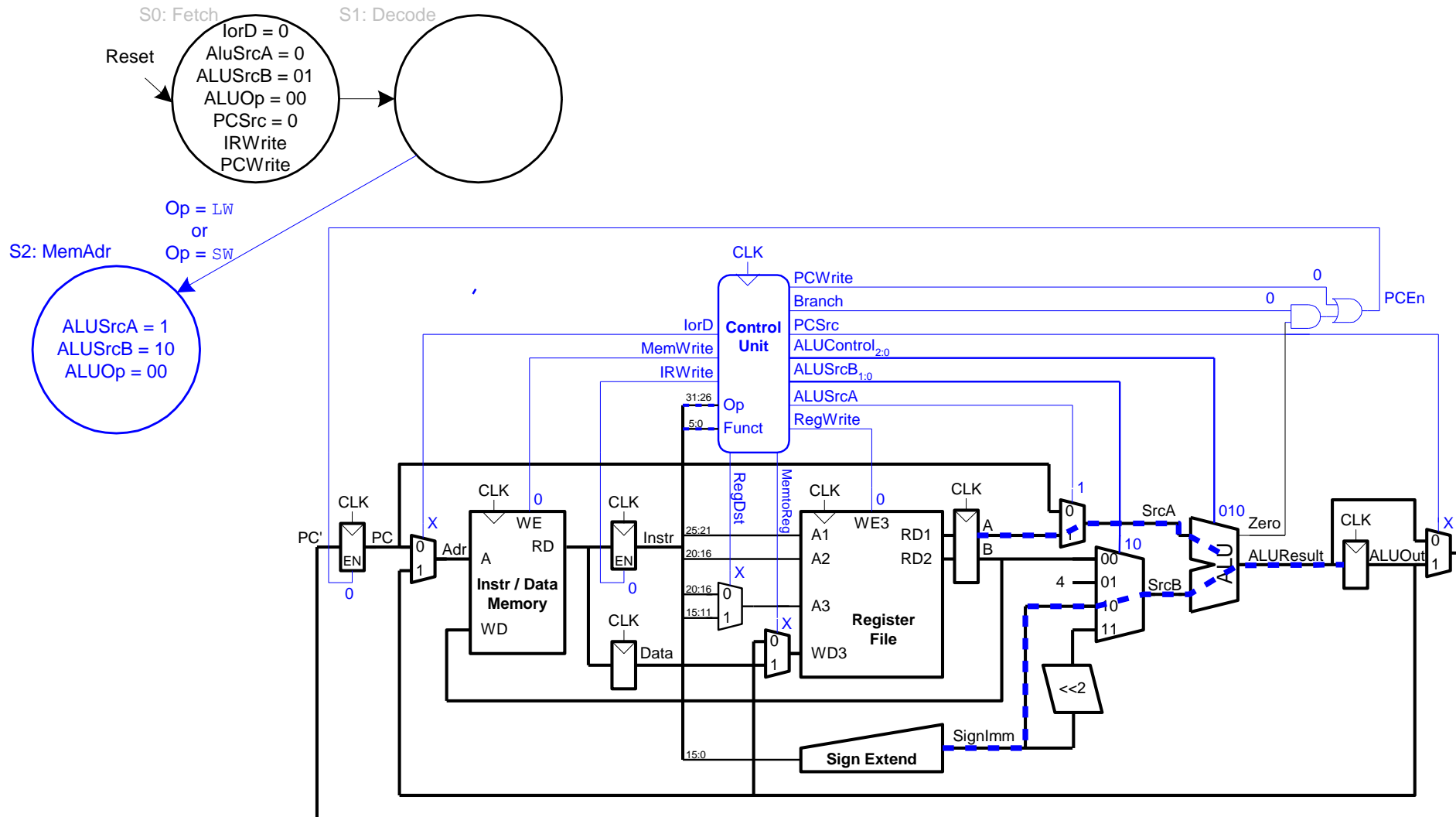


Main Controller FSM: lw

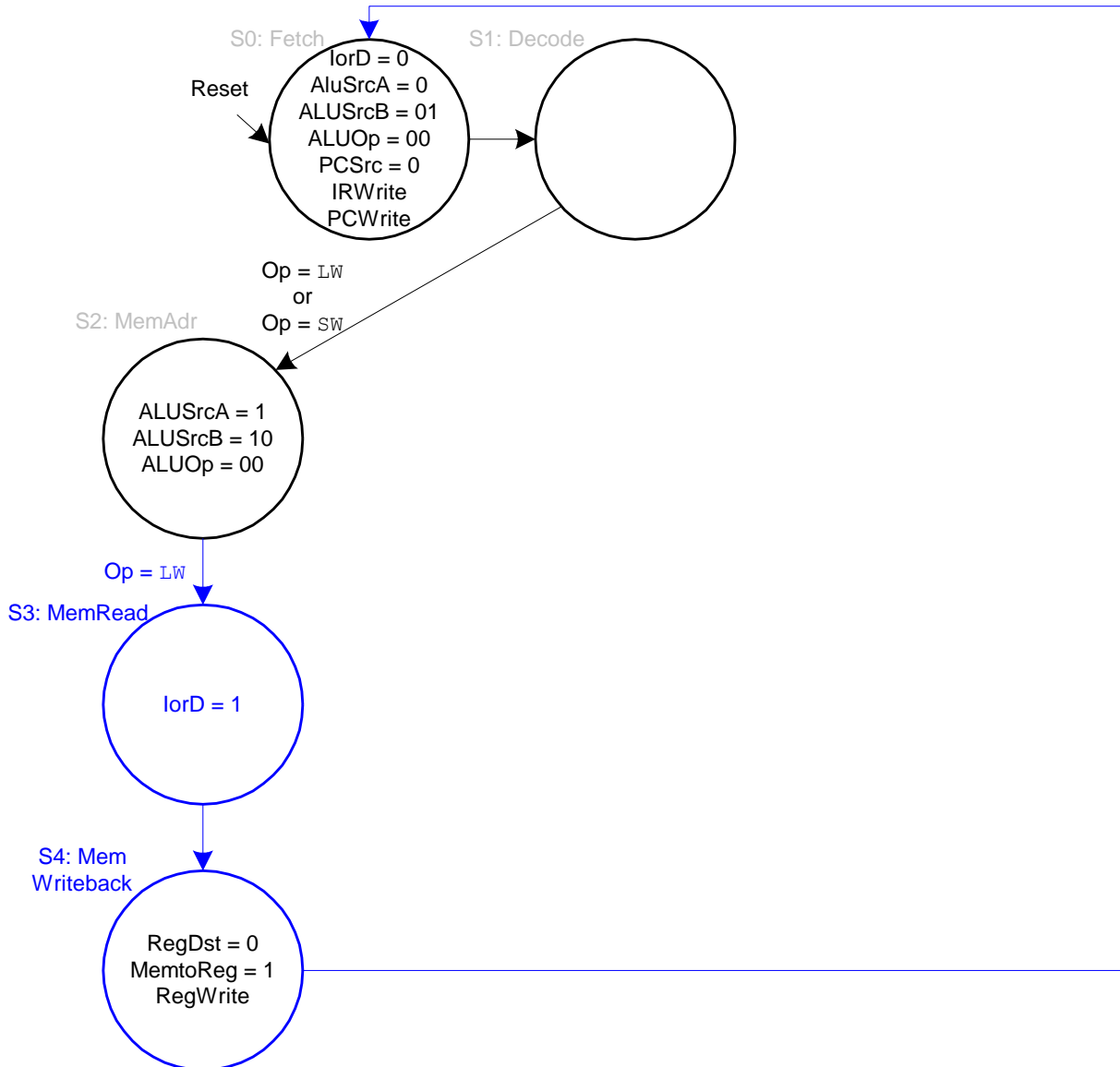


Main Controller FSM: sw

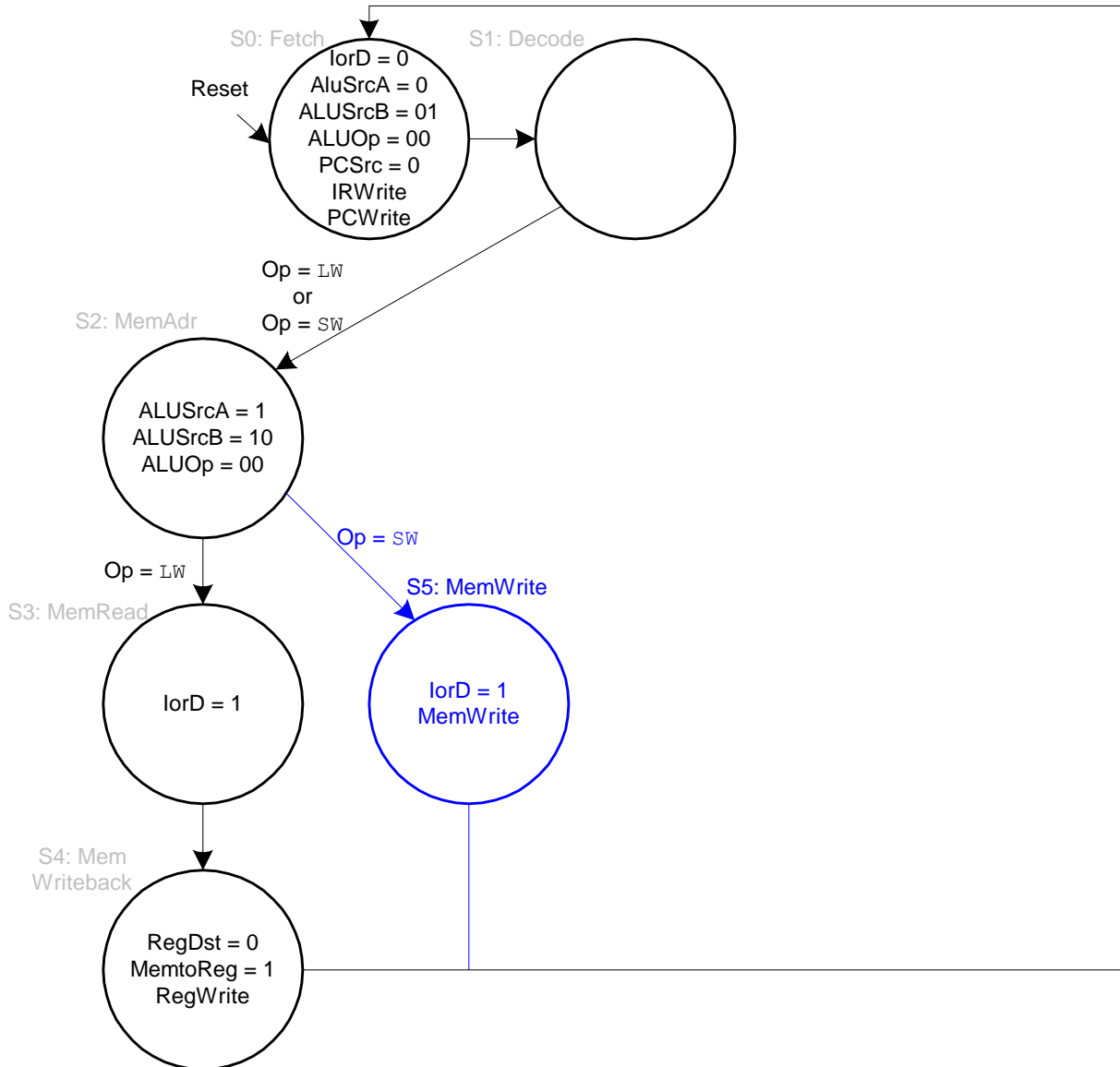


Main Controller FSM: R-Type

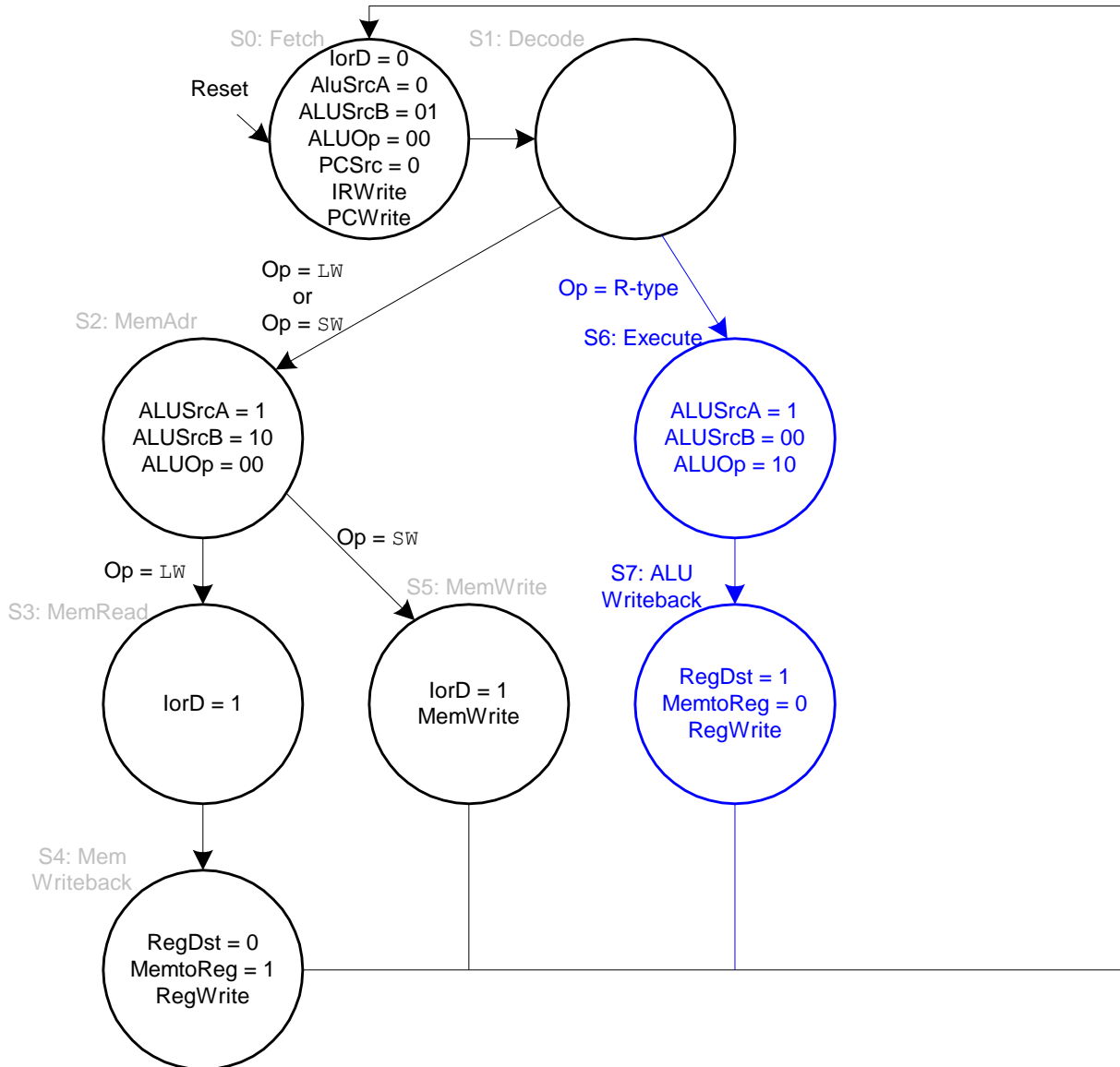


Main Controller FSM: beq

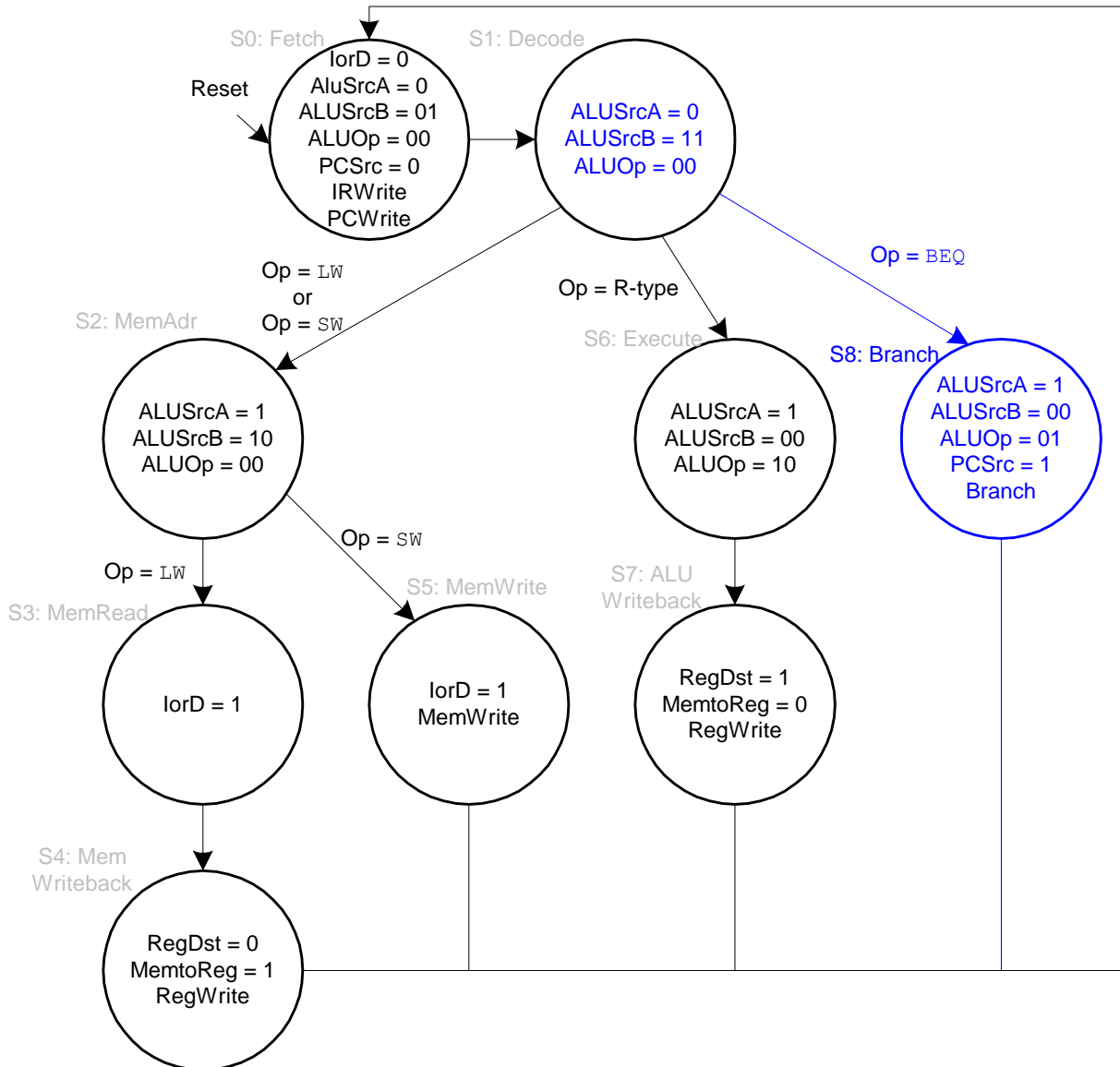


Complete Multi-cycle Controller FSM

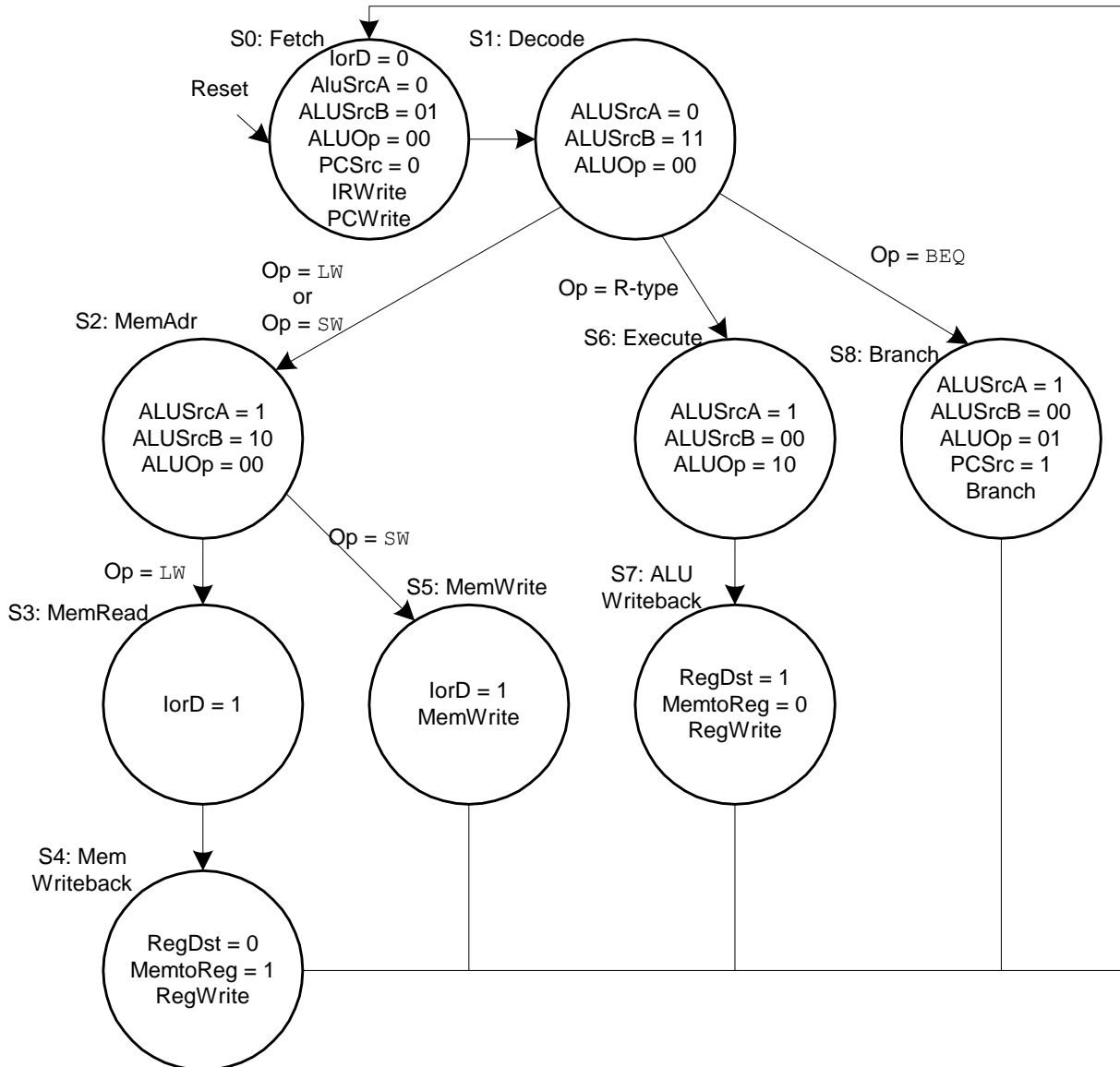


Main Controller FSM: addi

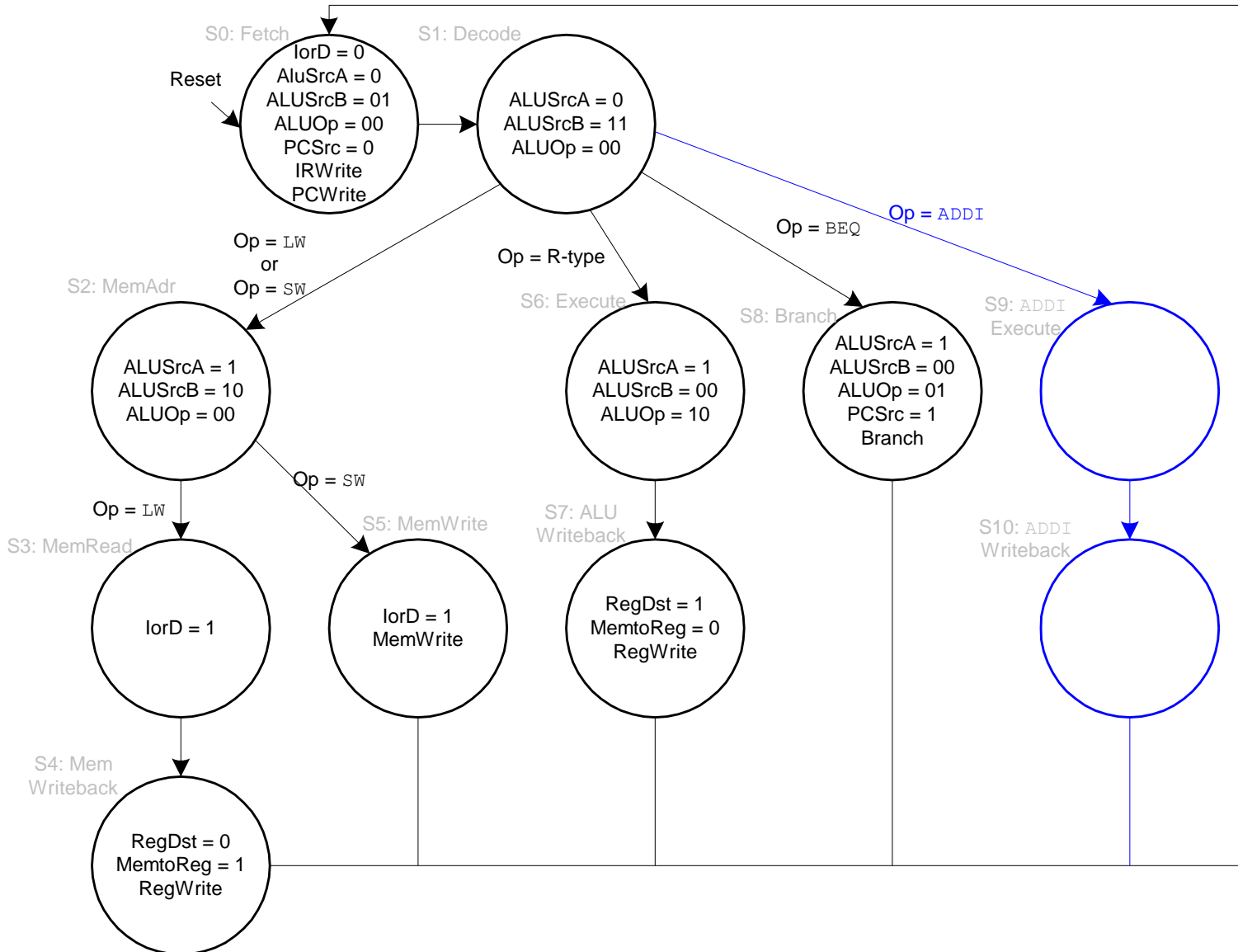


Main Controller FSM: addi

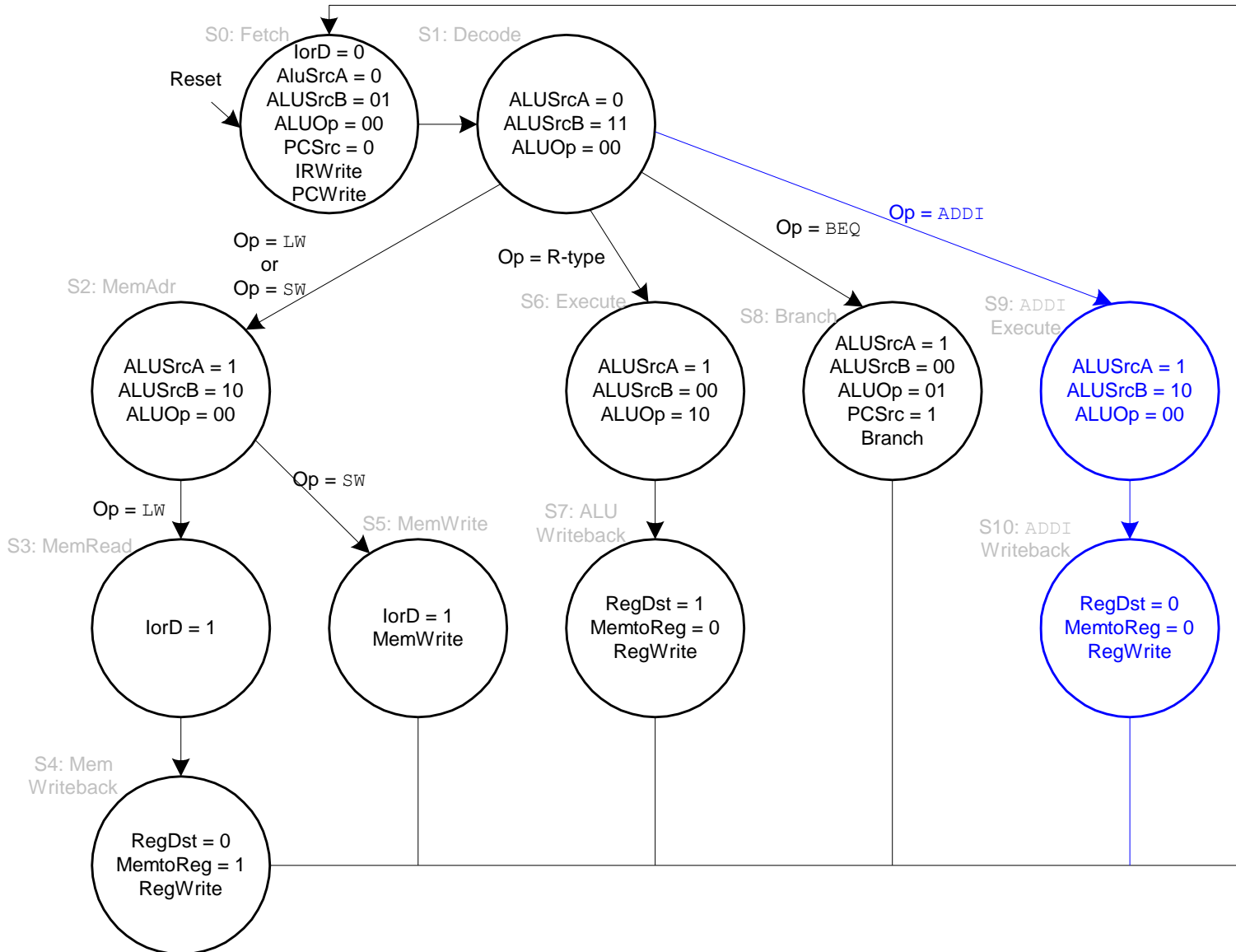


Extended Functionality: j

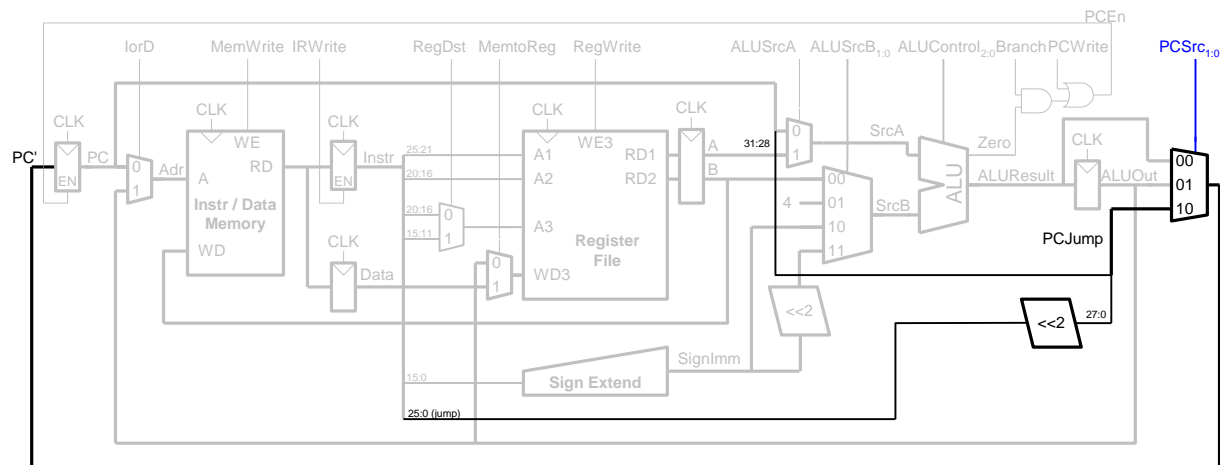

Control FSM: j

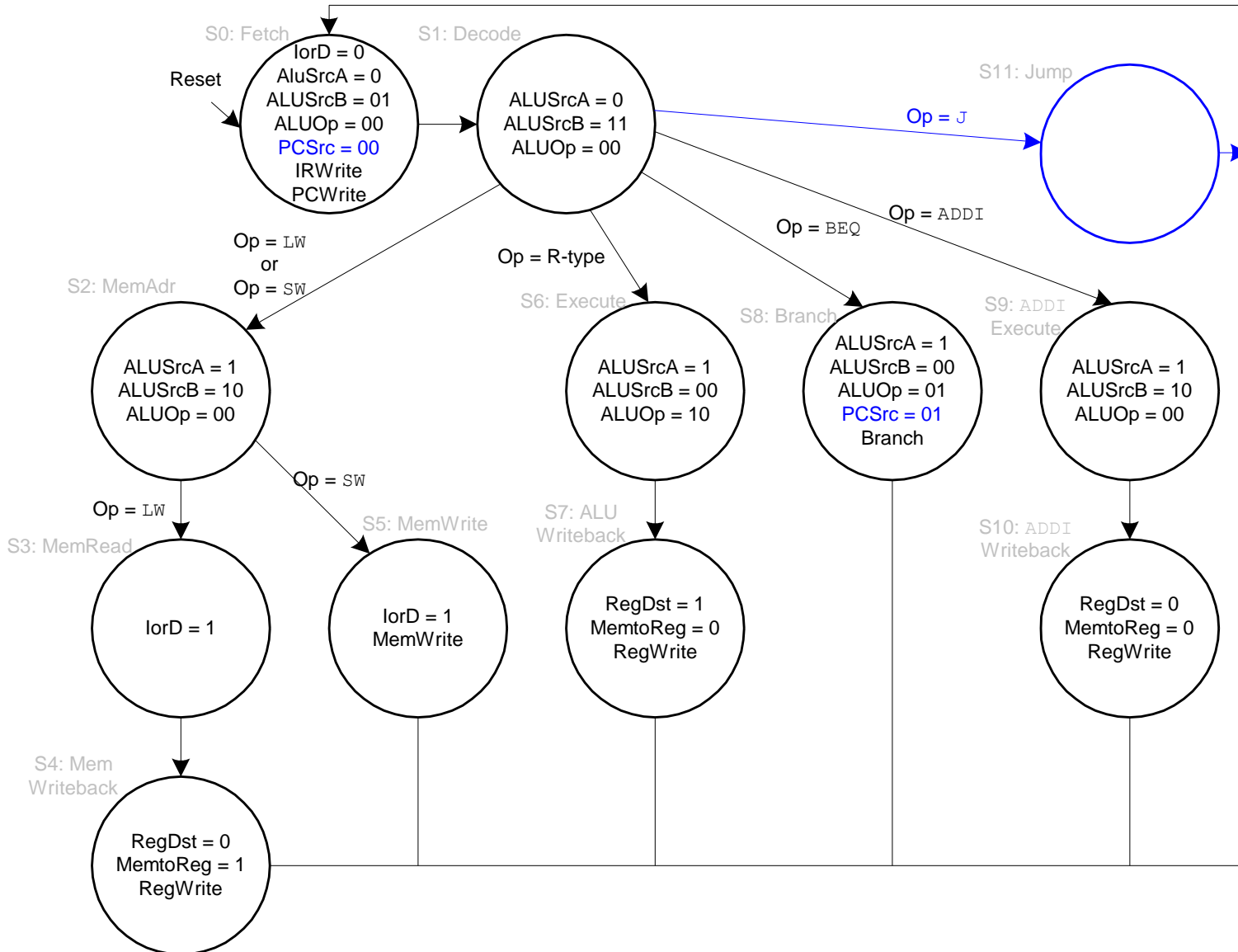

Control FSM: j

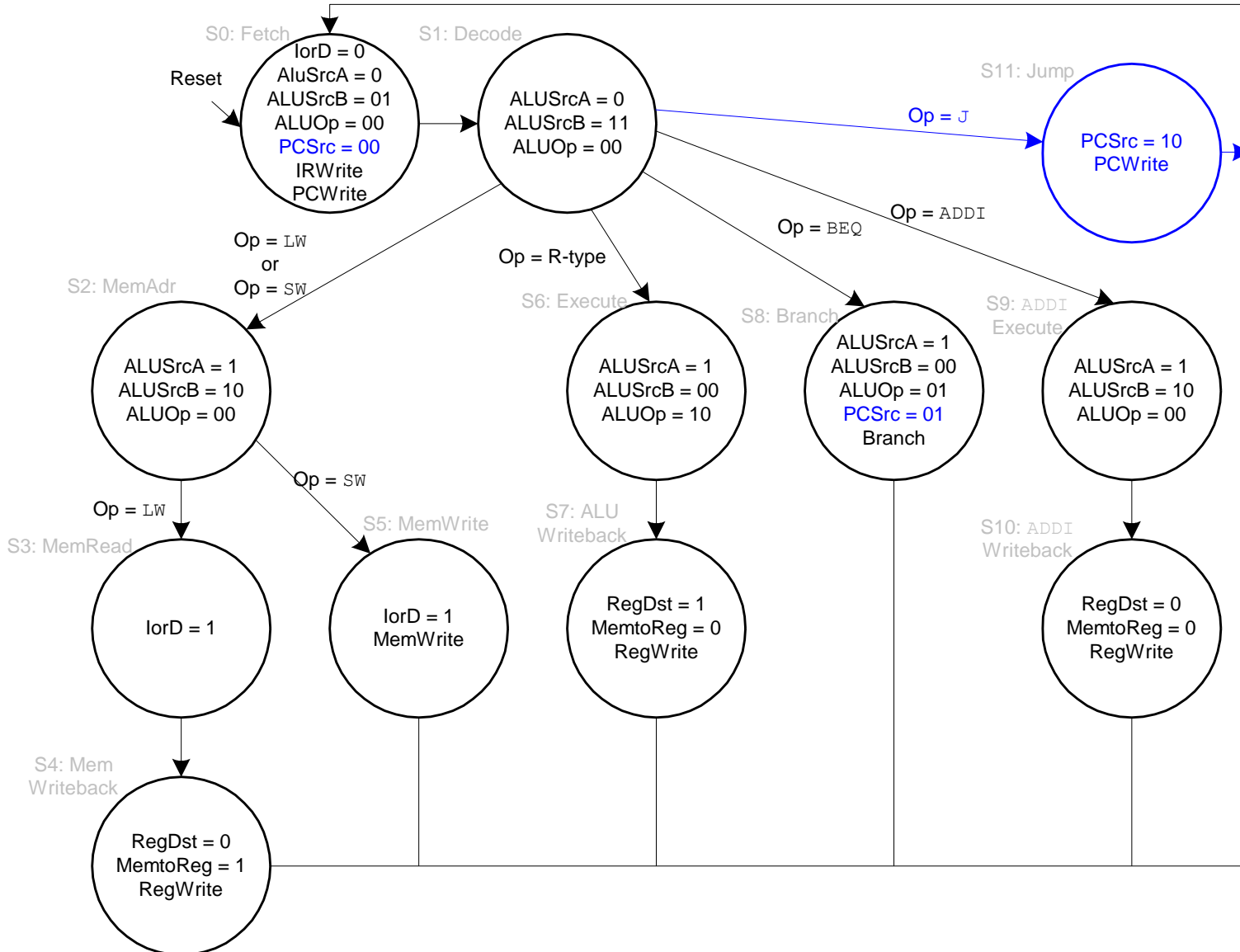


Multi-cycle Performance

- **Instructions take different number of cycles:**
 - 3 cycles: beq, j
 - 4 cycles: R-Type, sw, addi
 - 5 cycles: lw
- **CPI is weighted average, i.e. SPECINT2000 benchmark:**
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type
- ***Average CPI*** = $(0.11 + 0.02) 3 + (0.52 + 0.10) 4 + (0.25) 5$
= 4.12

Multi-cycle Performance

■ Multi-cycle critical path:


$$T_c =$$

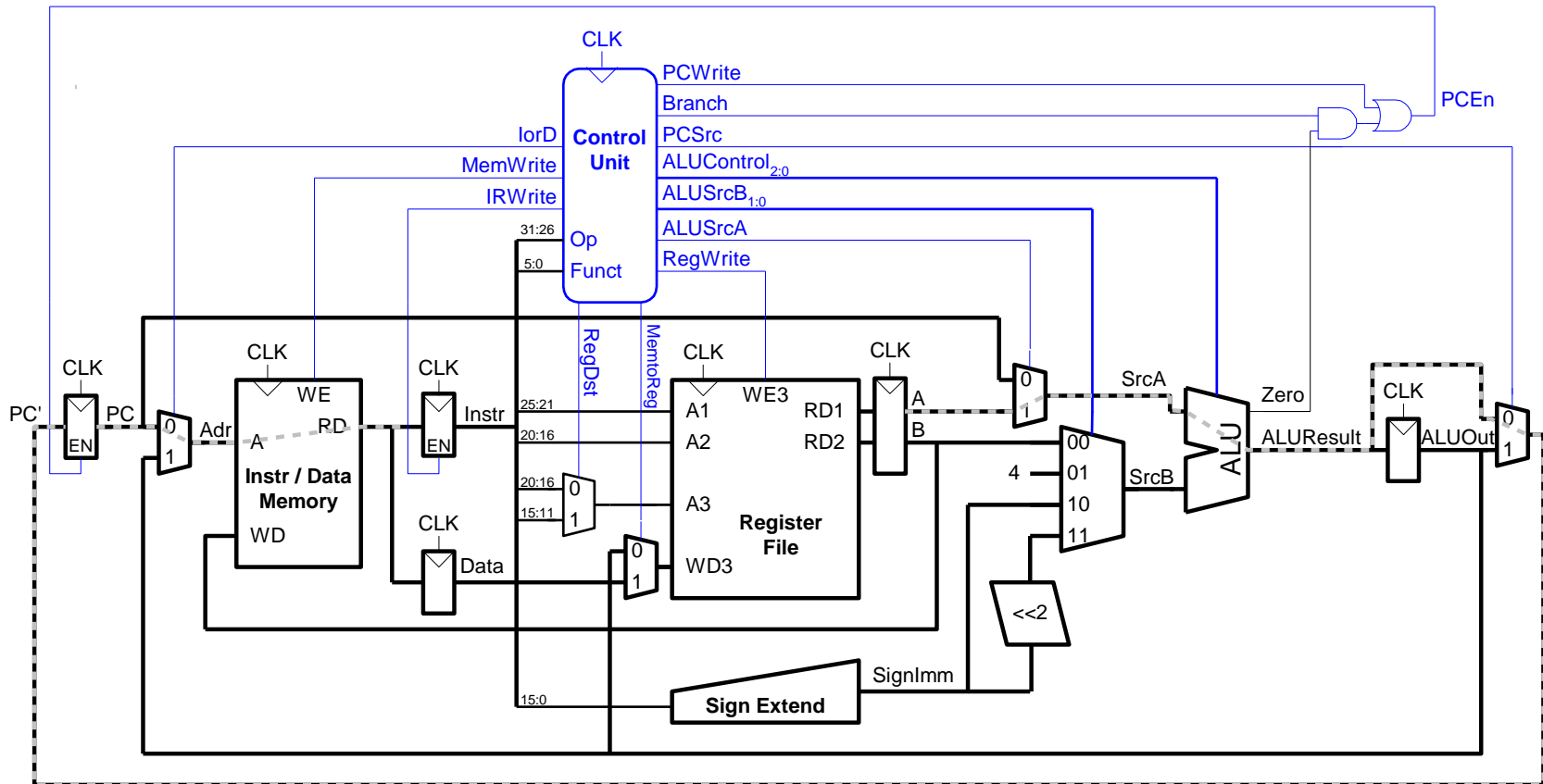

Multi-cycle Performance

■ Multicycle critical path:
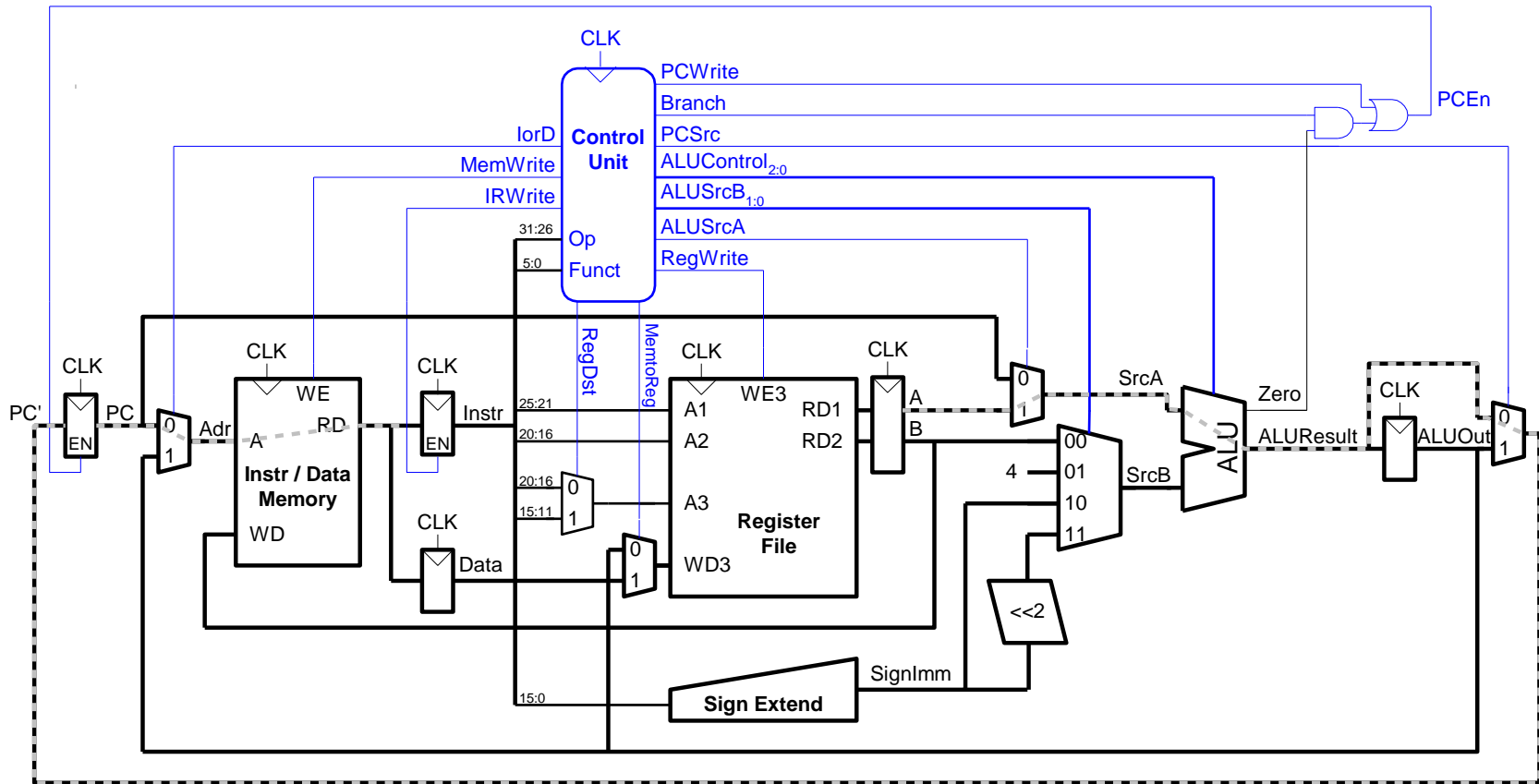
$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Multicycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

T_c =

Multicycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

$$\begin{aligned}T_c &= t_{pcq_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\&= [30 + 25 + 250 + 20] \text{ ps} \\&= 325 \text{ ps}\end{aligned}$$


Multi-cycle Performance Example

- For a program with 100 billion instructions executing on a multi-cycle MIPS processor
 - $CPI = 4.12$
 - $T_c = 325 \text{ ps}$
- **Execution Time** $= (\# \text{ instructions}) \times CPI \times T_c$
 $= (100 \times 10^9)(4.12)(325 \times 10^{-12})$
 $= 133.9 \text{ seconds}$
- This is slower than the single-cycle processor (92.5 seconds). Why?


Multi-cycle Performance Example

- For a program with 100 billion instructions executing on a multi-cycle MIPS processor
 - $CPI = 4.12$
 - $T_c = 325 \text{ ps}$
- **Execution Time** $= (\# \text{ instructions}) \times CPI \times T_c$
 $= (100 \times 10^9)(4.12)(325 \times 10^{-12})$
 $= 133.9 \text{ seconds}$
- This is slower than the single-cycle processor (92.5 seconds).
Why?
 - Not all steps the same length
 - Sequencing overhead for each step ($t_{pcq} + t_{setup} = 50 \text{ ps}$)

Review: Single-Cycle MIPS Processor

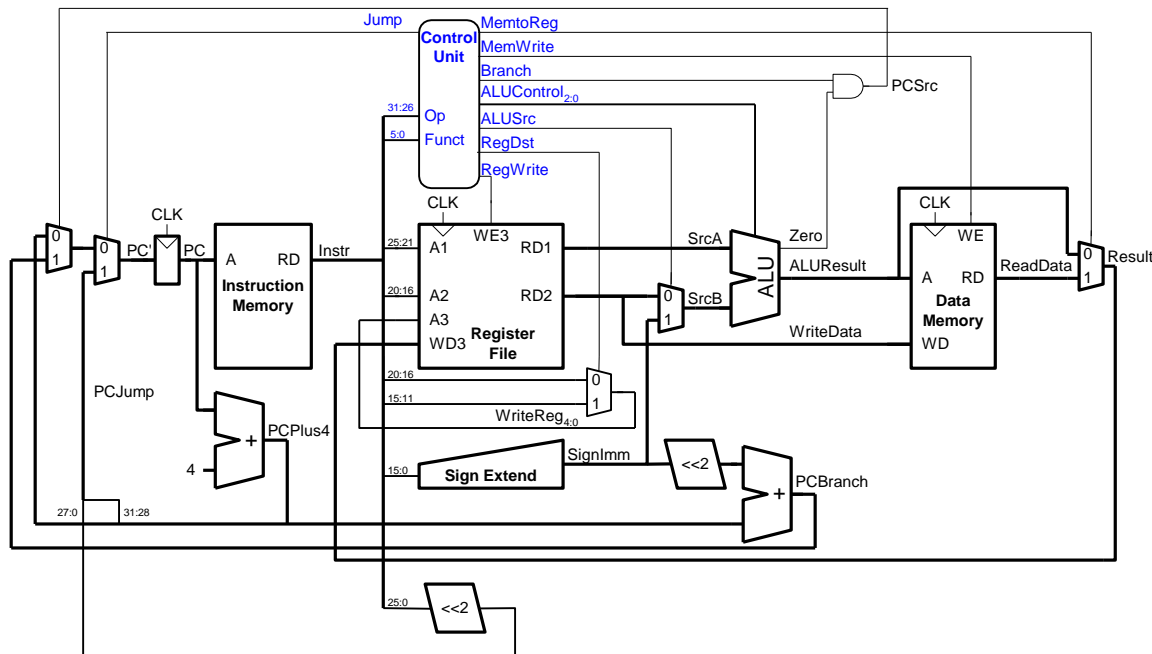

Review: Multicycle MIPS Processor

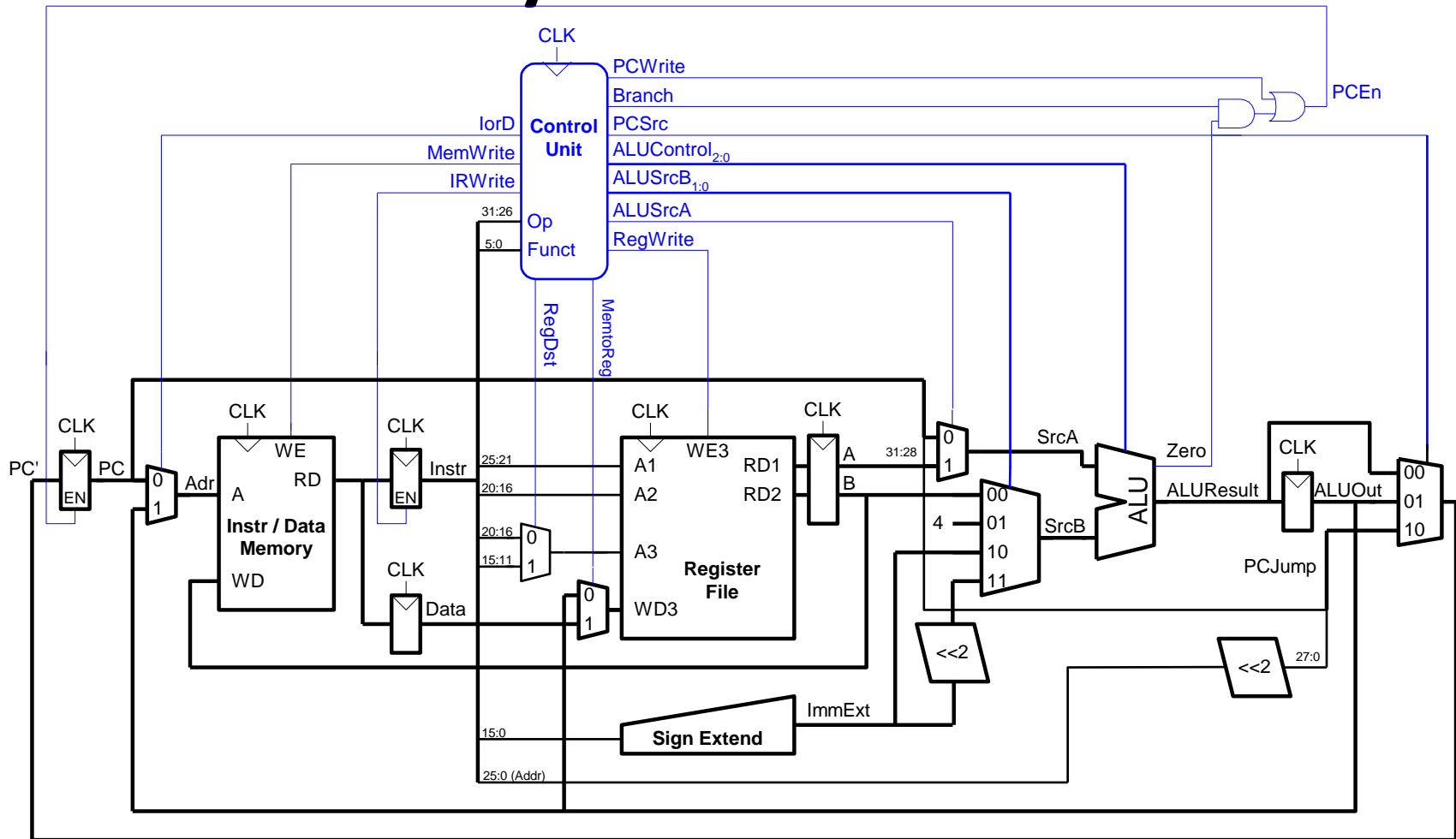

What Have We Learned?

- **A more 'realistic' architecture**
 - Shared data and program memory
 - A single ALU for all operations
- **Multi-cycle: Operations take different number of cycles**
 - Simpler operations take less steps
 - More complex operations take more steps
 - Average CPI
- **Bottom line**
 - Smaller
 - More complex control
 - Not necessarily faster (overhead)